

## Solutions to Chapter 7:

### Exercise 7.1: Buck Converter

- a) See Figure 7.4.
- Capacitor  $C_1$ : In case of a solar module at the input the capacitor serves as a buffer storage for the solar energy.
  - Mosfet: Serves as a fast, wear-free and controllable switch
  - Choke coil  $L$ : Ensures a continuous current at the output
  - Capacitor  $C_2$ : Serves to smooth the output voltage
  - Diode  $D$ : Flyback diode, which enables that the current can continuously flow even when the Mosfet is switched off
- b) In case of a high switching frequency small inductors and capacitors can be used without running into the undesired discontinuous mode.
- c) High switching frequencies cause higher switching losses. Therefore suitable fast, low-loss switches (e.g. of silicon-carbide) should be used.

### Exercise 7.2: Feed-In Variations

See Figures 7.8 und 7.9.

### Exercise 7.3: Inverter Variations

- a) See Section 7.2.2.
- b) The Current curve is almost exactly sinusoidal and therefore enhances the quality of the grid voltage.
- c) i) In the case of thin film modules.  
ii) In the case of special c-Si modules (e.g. Sunpower, Evergreen) that can be prone to PID.  
iii) In the case of all modules, which are not explicitly approved for the operation with inverters without transformers.
- d) It is used when a galvanic isolation is desired and one simultaneously wants to prevent the disadvantages of an inverter with mains transformer (poor efficiency, high weight etc.).
- e) i) The grid is symmetrically supplied.  
ii) The momentary value of the fed-in power is nearly constant so that only small storage capacitors are necessary in the inverter.  
iii) Two additional switching elements (50 % more) facilitate 200 % more power.

### Exercise 7.4: Inverter Dimensioning

Data from Table 6.1 and 7.2 as well from Figure 7.22:

#### Solar module:

$$\begin{aligned} V_{OC} &= 29.7 \text{ V}, & V_N &= 24.4 \text{ V} \\ I_{SC} &= 8.7 \text{ A}, & I_N &= 8.1 \text{ A} \\ P_N &= 200 \text{ Wp} & TC_U &= -0.34 \text{ \%/K} \end{aligned}$$

#### Inverter:

$$\begin{aligned} V_{DC\_N} &= 350 \text{ V}, & V_{MPP} &= 333 \text{ to } 500 \text{ V} \\ V_{Inv\_Max} &= 700 \text{ V}, & I_{Inv\_Max} &= 25 \text{ A} \\ P_{DC\_N} &= 8.25 \text{ kW}, & P_{AC\_N} &= 8 \text{ kW} \end{aligned}$$

- a)  $V_{OC_{(-10^\circ C)}} \approx V_{OC} \cdot [1 + TC_U \cdot (\vartheta - \vartheta_{STC})] = 29.7 \text{ V} \cdot [1 - 0.34 \text{ \%/K} \cdot (-10^\circ \text{C} - 25^\circ \text{C})] = \underline{33.2 \text{ V}}$
- $$n_{Max} = \frac{U_{Inv\_Max}}{V_{OC_{(-10^\circ C)}}} = \frac{700 \text{ V}}{33.2 \text{ V}} = 21.1 = \underline{21 \text{ modules}}$$
- b)  $V_{MPP\_Modu(70^\circ C)} \approx V_{MPP} \cdot [1 + TC_U \cdot (\vartheta - \vartheta_{STC})] = 24.4 \text{ V} \cdot [1 - 0.34 \text{ \%/K} \cdot (70^\circ \text{C} - 25^\circ \text{C})] = \underline{20.7 \text{ V}}$
- $$n_{Min} = \frac{V_{MPP\_Min}}{V_{MPP\_Modu(70^\circ C)}} = \frac{333 \text{ V}}{20.7 \text{ V}} = 16.1 = \underline{17 \text{ modules}}$$
- c)  $n_{String\_Max} = \frac{I_{Inv\_Max}}{I_{String\_Max}} = \frac{I_{Inv\_Max}}{1.25 \cdot I_{MPP}} = \frac{25 \text{ A}}{1.25 \cdot 8.1 \text{ A}} = 2.5 = \underline{2 \text{ strings}}$

Thus, minimum 1 x 17 modules and maximum 2 x 21 = 42 modules can be installed.

- d) With regard to the power dimensioning a design factor of maximum 1 is recommended. With Equation (7.21) this leads to:

$$\Rightarrow P_{STC} \leq 1 \cdot P_{AC\_N} = 8 \text{ kW}$$

Therefore, the optimal plant configuration comprises two strings with 20 modules each. Possible were also 19 per string or - if necessary - 21 modules per string.